

Automotive Technology
Wiring Diagram Practice Maze VI

Name _____ Date _____ Period _____

Solve the maze using a highlighter marker making no mistakes!

