

Chapter 18

Circuit Types and Ohm's Law



Name _____

Date _____


Instructor _____

Score _____

Objective: After studying this chapter, you will be able to compare the operating characteristics of series, parallel, and series-parallel circuits and explain the operation of a frame-ground circuit.

Circuit Types

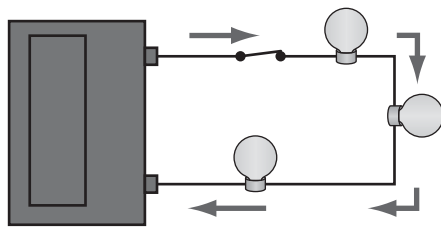1. A(n) _____ is a closed electrical path for current.
2. Identify the circuit types illustrated below.




A


(A) _____

(B) _____

(C) _____

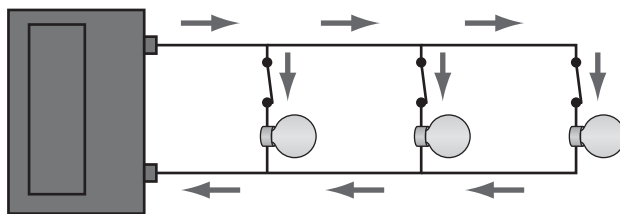

B

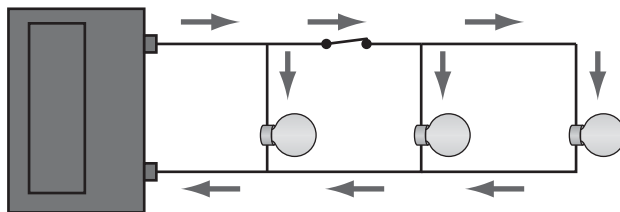

C

3. A(n) _____ circuit has only one path for current.

4. If a string of lights is wired in _____, one burned-out _____ bulb will not affect the operation of the other bulbs in the circuit.

_____ 5. A frame-ground circuit uses the vehicle's _____ to return electricity to the power source.
(A) metal structure
(B) windshield
(C) electrical system
(D) tires

6. Explain *conventional current theory*.

7. Which battery cable is bolted to the vehicle frame to allow the metal structure of the vehicle to serve as a large conductor to carry current?

8. The wire that carries current to the load is the _____ wire. _____

9. The _____ is the part of the circuit between the load _____ and the negative terminal of the battery.

Ohm's Law

10. Define *Ohm's law*.

11. Name the three formulas that represent Ohm's law.

_____ 12. A change in _____ affects the amount of current in a circuit.
(A) resistance
(B) voltage
(C) Both A and B.
(D) None of the above.

13. Most automotive electrical problems are caused _____ by a change in circuit _____.

Name _____

Circuit Calculations

14. Name the three general rules that apply to a series circuit.

15. Name the three basic rules of parallel circuit calculations.

16. The ____ of a number equals 1 divided by that number. _____

17. In a series-parallel circuit, you can find the total resistance of the circuit by calculating the resistance of each parallel section and then adding the series resistances to these values to obtain a single ____ resistance.

_____ 18. The unit of measure for electric power is the ____.
(A) amp
(B) volt
(C) watt
(D) ohm

19. What is the formula for power?

_____ 20. Power ratings for hybrid motor-generators and HV batteries can be given in ____.
(A) amps
(B) volts
(C) ohms
(D) kilowatts

21. Vehicle batteries may have a watt rating to indicate their ____ potential. _____

22. To avoid having to read and write large numbers representing electrical values, ____ are used with these values to indicate a multiplier, or exponent, of the value. _____

23. One ____ equals 1000 Ω . _____

24. How many ohms are indicated by 5 MΩ?

- _____ 25. Which of the following is *not* one of the most commonly used prefixes in automotive electronics?
- (A) milli
 - (B) exa
 - (C) kilo
 - (D) micro